22) Use Kirchhoff's rules to solve for the current through each of the resistors R_1, R_2 and R_3.

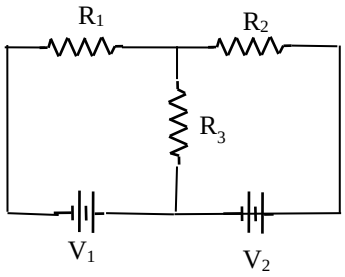

$V_1 = 12$ V
$V_2 = 9$ V

$R_1 = 7\ \Omega$
$R_2 = 8\ \Omega$
$R_3 = 4\ \Omega$